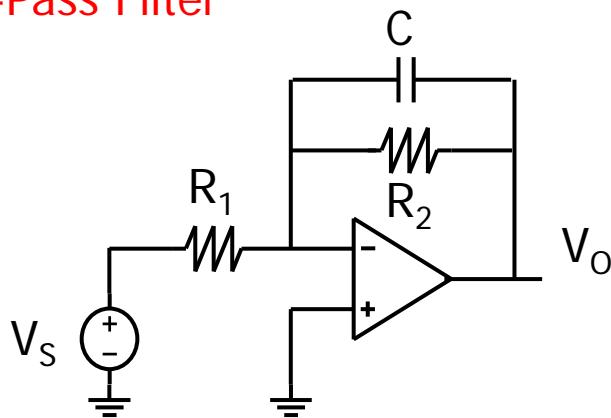


LAB 5 (1)

Low-Pass Filter




At **low** frequency,


$$\frac{V_o}{V_s}(\omega) \approx -\frac{R_2}{R_1}$$

At **high** frequency,
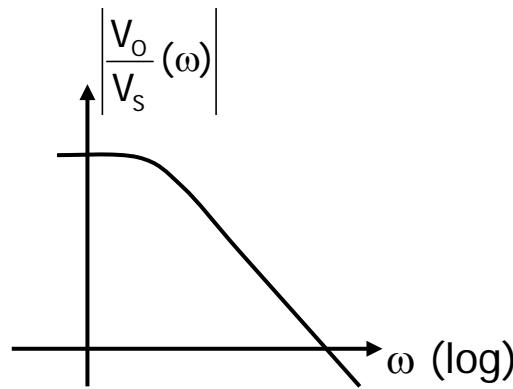
$$\frac{V_o}{V_s}(\omega) \approx -\frac{1}{j\omega CR_1}$$



High-Pass Filter

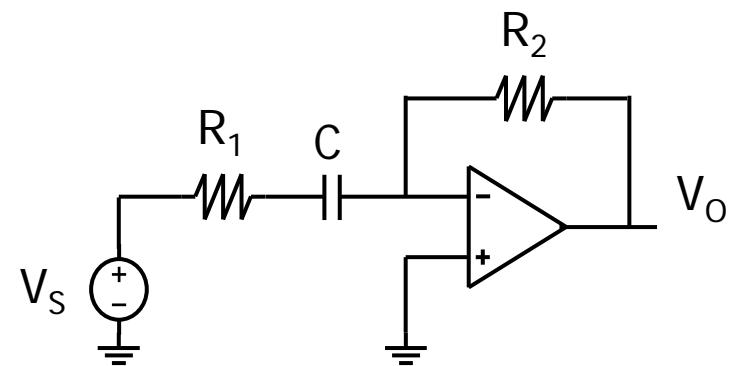


At **low** frequency,



$$\frac{V_o}{V_s}(\omega) \approx -j\omega CR_2$$

At **high** frequency,
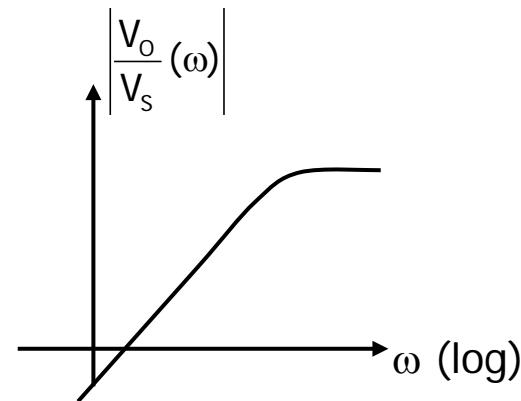
$$\frac{V_o}{V_s}(\omega) \approx -\frac{R_2}{R_1}$$



LAB 5 (2)

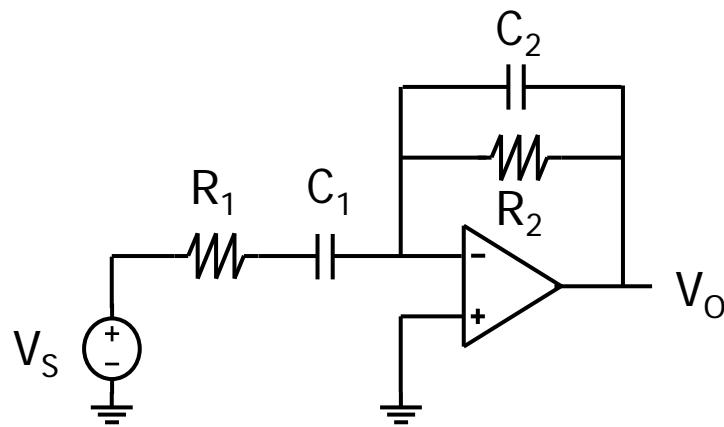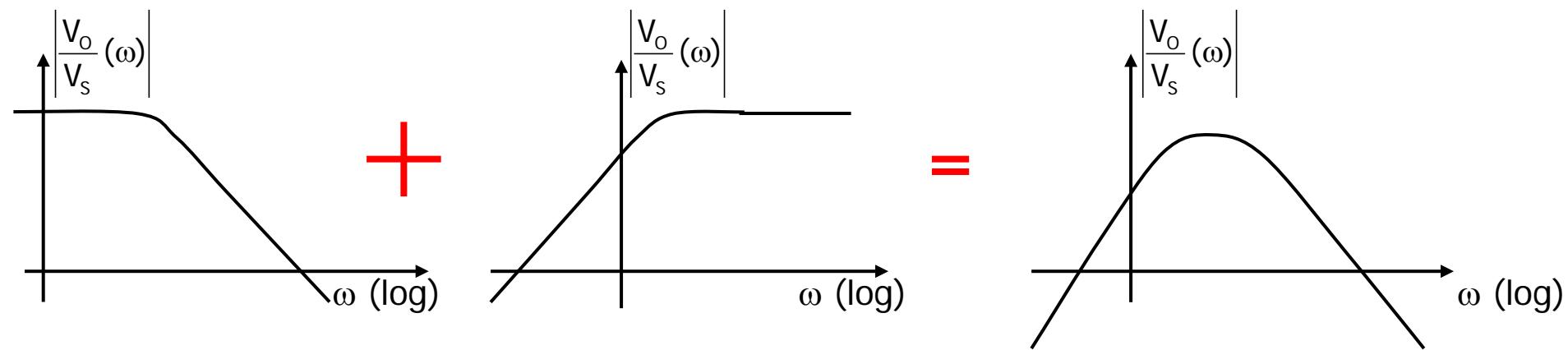

At **low** frequency,


$$\frac{V_o}{V_s}(\omega) \approx -j\omega C_1 R_2$$

At **high** frequency,

$$\frac{V_o}{V_s}(\omega) \approx -j\omega C_2 R_1$$

LAB 5 (3)

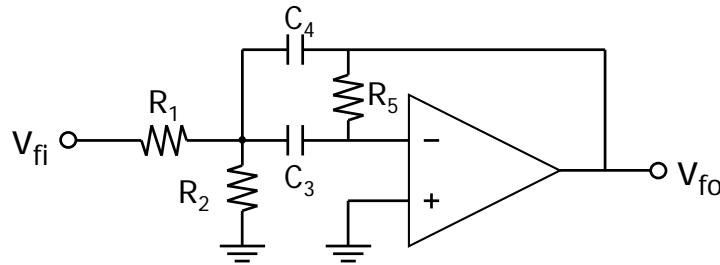In Lab 5, a multiple-feedback is used to implement the band-pass filter.



$$\frac{V_{fo}}{V_{fi}} = \frac{-s\left(\frac{1}{R_1 C_4}\right)}{s^2 + s\left(\frac{1}{R_5}\right)\left(\frac{1}{C_3} + \frac{1}{C_4}\right) + \left(\frac{1}{R_5 C_3 C_4}\right)\left(\frac{1}{R_1} + \frac{1}{R_2}\right)}$$


With $R_2 \gg R_1$ and $C_3 = C_4 = C$,

$$\frac{V_{fo}}{V_{fi}} \approx \frac{-s\left(\frac{1}{R_1 C}\right)}{s^2 + s\left(\frac{2}{R_5 C}\right) + \left(\frac{1}{R_1 R_5 C^2}\right)}$$

Compare the quadratic equation of $s^2 + \frac{s\omega_0}{Q} + \omega_0^2$

gives
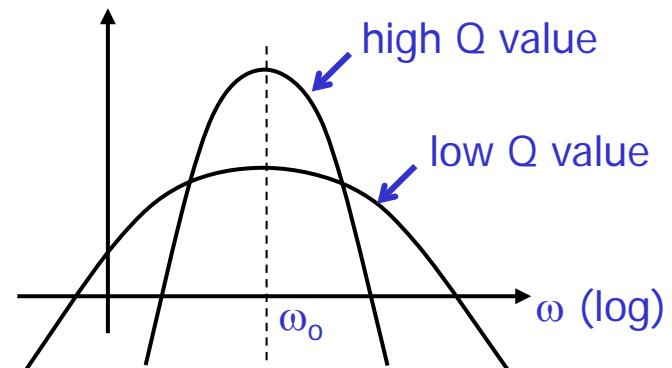
$$\omega_0 = \frac{1}{\sqrt{R_5 R_1 C}} \quad \text{and} \quad Q = \frac{1}{2} \sqrt{\frac{R_5}{R_1}}$$



Three-Band Audio Equalizer:

- Use an adder to combine the output of 3 band-pass filters (BPF1 to BPF3)
- Need to design each band-pass filter with different ω_0 and Q value to optimize the performance of the equalizer
- An average human can usually receive audible frequencies from 20Hz to 20kHz.

